

Name:

Student ID #:

Date:

US 29440 v1 Theory

Question 12

Draw a simple switchboard schematic diagram using standard symbols and with sufficient detail to enable unique identification of all items necessary for installation of the circuit in an enclosure. It should include a three phase motor-starter with protection to include a push button and PLC.